

Physics 1214 - General Physics II

Quiz #16 - 2013.02.27

Name: _____

1. What relationship must be satisfied for a series $R-L-C$ circuit to experience resonance?

2. What is the difference between current in a series $R-L-C$ circuit and parallel $R-L-C$ circuit at resonance?