

Physics 1214 - General Physics II

Quiz #6 - 2013.02.01

Name: _____

1. How is the equivalent resistance of a pair of resistors in series related to the individual resistances? What about if the resistors are in parallel?

2. State both Kirchhoff's Junction (Point) Rule, as well as Kirchhoff's Loop Rule.